



# Digital Logic Design

---

- Basics
- Combinational Circuits
- Sequential Circuits

Pu-Jen Cheng

Adapted from the slides prepared by S. Dandamudi for the book,  
Fundamentals of Computer Organization and Design.




# Introduction to Digital Logic Basics

---

- Hardware consists of a few simple building blocks
  - These are called *logic gates*
    - AND, OR, NOT, ...
    - NAND, NOR, XOR, ...
- Logic gates are built using transistors
  - NOT gate can be implemented by a single transistor
  - AND gate requires 3 transistors
- Transistors are the fundamental devices
  - Pentium consists of 3 million transistors
  - Compaq Alpha consists of 9 million transistors
  - Now we can build chips with more than 100 million transistors

 
# Basic Concepts

- Simple gates
  - AND
  - OR
  - NOT
- Functionality can be expressed by a truth table
  - A truth table lists output for each possible input combination
- Precedence
  - NOT > AND > OR
  - $F = A \bar{B} + \bar{A} B$   
 $= (A (\bar{B})) + ((\bar{A}) B)$




AND gate

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

 

OR gate

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

 

NOT gate


A	F
0	1
1	0

Logic symbol

Truth table

 
# Basic Concepts (cont.)

- Additional useful gates
  - NAND
  - NOR
  - XOR
- $\text{NAND} = \text{AND} + \text{NOT}$
- $\text{NOR} = \text{OR} + \text{NOT}$
- XOR implements exclusive-OR function
- NAND and NOR gates require only 2 transistors
  - AND and OR need 3 transistors!



NAND gate

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

 

NOR gate

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0



XOR gate

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

Logic symbol

Truth table



## Basic Concepts (cont.)

---

- Number of functions
  - With  $N$  logical variables, we can define  $2^{2^N}$  functions
  - Some of them are useful
    - AND, NAND, NOR, XOR, ...
  - Some are not useful:
    - Output is always 1
    - Output is always 0
  - “Number of functions” definition is useful in proving completeness property



# Basic Concepts (cont.)

---

- Complete sets

- A set of gates is complete

- If we can implement any logical function using only the type of gates in the set

- You can use as many gates as you want

- Some example complete sets

- {AND, OR, NOT} ← Not a minimal complete set

- {AND, NOT}

- {OR, NOT}

- {NAND}


- {NOR}

- Minimal complete set


- A complete set with no redundant elements.
 
# Basic Concepts (cont.)


- Proving NAND gate is universal
- NAND gate is called *universal gate*



AND gate

 


NOT gate

 


OR gate
 
# Basic Concepts (cont.)


- Proving NOR gate is universal
- NOR gate is called *universal gate*



OR gate

 


NOT gate

 


AND gate




 


# Logic Chips

 


7400

 


7408

 


7432

 


7404

 


7486

 

7402

 

7420

 

7430



# Logic Chips (cont.)

---

- Integration levels
  - SSI (small scale integration)
    - Introduced in late 1960s
    - 1-10 gates (previous examples)
  - MSI (medium scale integration)
    - Introduced in late 1960s
    - 10-100 gates
  - LSI (large scale integration)
    - Introduced in early 1970s
    - 100-10,000 gates
  - VLSI (very large scale integration)
    - Introduced in late 1970s
    - More than 10,000 gates



# Logic Functions

---

- Logical functions can be expressed in several ways:
  - Truth table
  - Logical expressions
  - Graphical form
- Example:
  - Majority function
    - Output is 1 whenever majority of inputs is 1
    - We use 3-input majority function


# Logic Functions (cont.)

3-input majority function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


- Logical expression form

$$F = A B + B C + A C$$

 

 
# Logical Equivalence


- All three circuits implement  $F = A B$  function



(a)

 

(b)

 

(c)




# Logical Equivalence (cont.)

---

- Proving logical equivalence of two circuits
  - Derive the logical expression for the output of each circuit
  - Show that these two expressions are equivalent
    - Two ways:
      - You can use the truth table method
        - For every combination of inputs, if both expressions yield the same output, they are equivalent
        - Good for logical expressions with small number of variables
      - You can also use algebraic manipulation
        - Need Boolean identities
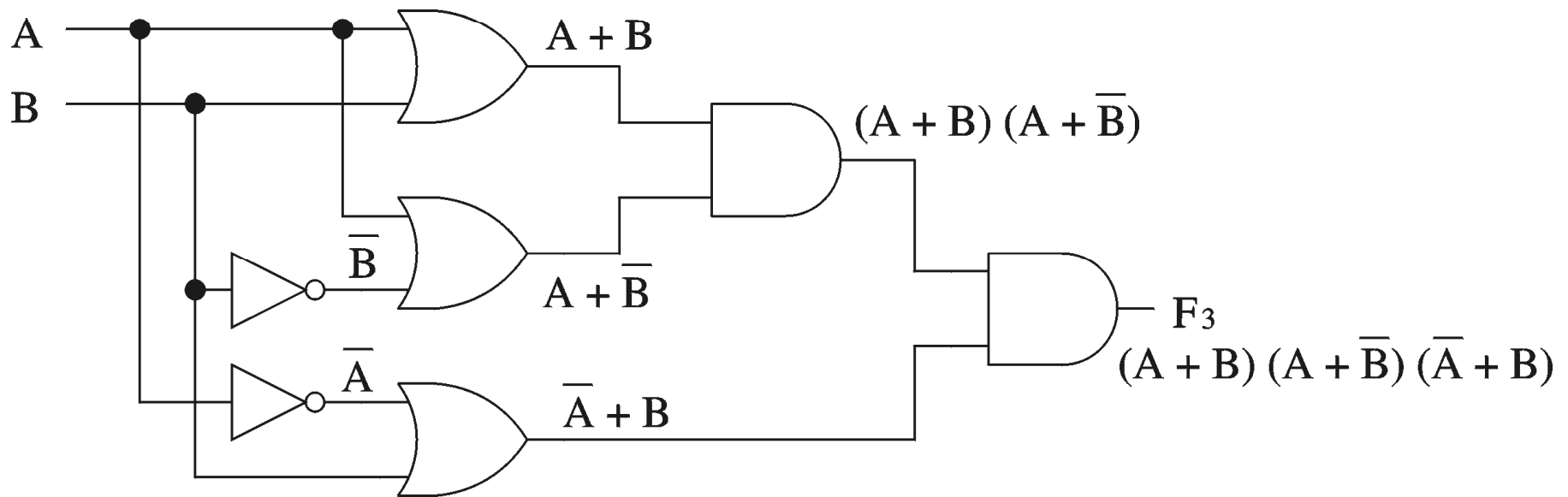
# Logical Equivalence (cont.)

- Derivation of logical expression from a circuit
  - Trace from the input to output
    - Write down intermediate logical expressions along the path





## Logical Equivalence (cont.)

---

- Proving logical equivalence: Truth table method

<b>A</b>	<b>B</b>	<b>F1 = A B</b>	<b>F3 = (A + B) (A + <math>\bar{B}</math>) (<math>\bar{A}</math> + B)</b>
<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>0</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>





# Boolean Algebra

## Boolean identities

<b>Name</b>	<b>AND version</b>	<b>OR version</b>
Identity	$x \cdot 1 = x$	$x + 0 = x$
Complement	$x \cdot \bar{x} = 0$	$x + \bar{x} = 1$
Commutative	$x \cdot y = y \cdot x$	$x + y = y + x$
Distribution	$x \cdot (y + z) = xy + xz$	$x + (y \cdot z) =$ $(x + y) (x + z)$
Idempotent	$x \cdot x = x$	$x + x = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$



# Boolean Algebra (cont.)

Name	AND version	OR version
Involution	$\overline{\overline{x}} = x$	---
Absorption	$x \cdot (x + y) = x$	$x + (x \cdot y) = x$
Associative	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	$x + (y + z) = (x + y) + z$
de Morgan	$\overline{x \cdot y} = \overline{x} + \overline{y}$	$\overline{x + y} = \overline{x} \cdot \overline{y}$



## Boolean Algebra (cont.)

---


- Proving logical equivalence: Boolean algebra method
  - To prove that two logical functions  $F1$  and  $F2$  are equivalent
    - Start with one function and apply Boolean laws to derive the other function
    - Needs intuition as to which laws should be applied and when
      - Practice helps
    - Sometimes it may be convenient to reduce both functions to the same expression
  - Example:  $F1 = A B$  and  $F3$  are equivalent
$$A B = (A + B) (A + \bar{B}) (\bar{A} + B)$$


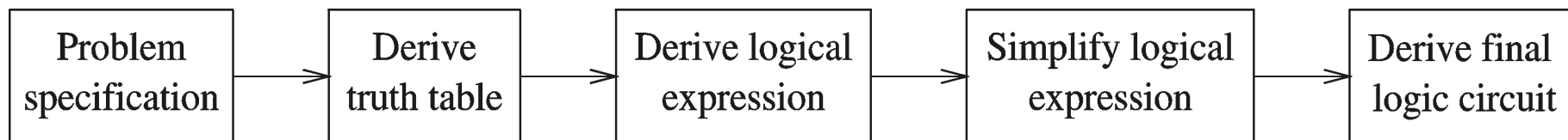
# Logic Circuit Design Process

---

- A simple logic design process involves
  - Problem specification
  - Truth table derivation
  - Derivation of logical expression
  - Simplification of logical expression
  - Implementation





# Deriving Logical Expressions

---

- Derivation of logical expressions from truth tables
  - sum-of-products (SOP) form
  - product-of-sums (POS) form
- SOP form
  - Write an AND term for each input combination that produces a 1 output
    - Write the variable if its value is 1; complement otherwise
  - OR the AND terms to get the final expression
- POS form
  - Dual of the SOP form

# Deriving Logical Expressions (cont.)

- 3-input majority function

<b>A</b>	<b>B</b>	<b>C</b>	<b>F</b>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- SOP logical expression

- Four product terms

➤ Because there are 4 rows with a 1 output

$$F = \overline{A} B C + A \overline{B} C + A B \overline{C} + A B C$$

# Deriving Logical Expressions (cont.)

- 3-input majority function

<b>A</b>	<b>B</b>	<b>C</b>	<b>F</b>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- POS logical expression

- Four sum terms

➤ Because there are 4 rows with a 0 output

$$F = (A + B + C) (A + B + \bar{C}) \\ (A + \bar{B} + C) (\bar{A} + B + C)$$



# Logical Expression Simplification

---

- Two basic methods
  - Algebraic manipulation
    - Use Boolean laws to simplify the expression
      - Difficult to use
      - Don't know if you have the simplified form
  - Karnaugh map (K-map) method
    - Graphical method
    - Easy to use
      - Can be used to simplify logical expressions with a few variables



# Algebraic Manipulation

- Majority function example

$$\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC =$$

$$\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC + \underbrace{ABC + ABC}_{\text{Added extra}}$$

- We can now simplify this expression as

$$BC + AC + AB$$

- A difficult method to use for complex expressions

# Karnaugh Map Method

Note the order

	B	0	1
A	0		
	1		

(a) Two-variable K-map

	BC	00	01	11	10
A	0				
	1				


(b) Three-variable K-map

	CD	00	01	11	10
AB	00				
	01				
	11				
	10				


(c) Four-variable K-map

# Karnaugh Map Method (cont.)

## Simplification examples

 


(a) Majority function

 

(b) Even-parity function


# Karnaugh Map Method (cont.)

First and last columns/rows are adjacent

 


# Karnaugh Map Method (cont.)

Minimal expression depends on groupings

 

(a)

 

(b)

# Karnaugh Map Method (cont.)

No redundant groupings

AB \ CD	00	01	11	10
00	0	0	1	0
01	1	1	1	0
11	0	1	1	1
10	0	1	0	0

(a) Nonminimal simplification


AB \ CD	00	01	11	10
00	0	0	1	0
01	1	1	1	0
11	0	1	1	1
10	0	1	0	0

(b) Minimal simplification

# Karnaugh Map Method (cont.)

 - Example

- Seven-segment display
- Need to select the right LEDs to display a digit





## Karnaugh Map Method (cont.)

Truth table for segment d

No	A	B	C	D	Seg.	No	A	B	C	D	Seg.
0	0	0	0	0	1	8	1	0	0	0	1
1	0	0	0	1	0	9	1	0	0	1	1
2	0	0	1	0	1	10	1	0	1	0	?
3	0	0	1	1	1	11	1	0	1	1	?
4	0	1	0	0	0	12	1	1	0	0	?
5	0	1	0	1	1	13	1	1	0	1	?
6	0	1	1	0	1	14	1	1	1	0	?
7	0	1	1	1	0	15	1	1	1	1	?



# Karnaugh Map Method (cont.)

Don't cares simplify the expression a lot

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	0	1
11	0	0	0	0
10	1	1	0	0

(a) Simplification with no don't cares

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	0	1
11	d	d	d	d
10	1	1	d	d

(b) Simplification with don't cares



# Implementation Using NAND Gates

---

- Using NAND gates
  - Get an equivalent expression

$$A B + C D = \overline{\overline{A B + C D}}$$

- Using de Morgan's law

$$A B + C D = \overline{\overline{A B} \cdot \overline{C D}}$$


- Can be generalized
  - Majority function

$$A B + B C + A C = \overline{\overline{A B} \cdot \overline{B C} \cdot \overline{A C}}$$

**Idea:** NAND Gates: Sum-of-Products, NOR Gates: Product-of-Sums

## Implementation Using NAND Gates (cont.)

- Majority function

 



# Introduction to Combinational Circuits

---

- Combinational circuits
  - Output depends only on the current inputs
- Combinational circuits provide a higher level of abstraction
  - Help in reducing design complexity
  - Reduce chip count
- We look at some useful combinational circuits


# Multiplexers

- Multiplexer

- $2^n$  data inputs
- $n$  selection inputs
- a single output

- Selection input determines the input that should be connected to the output


4-data input MUX

 

$S_1$	$S_0$	O
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$


# Multiplexers (cont.)

## 4-data input MUX implementation

 


# Multiplexers (cont.)

## MUX implementations

 


Majority function

 


Even-parity function

# Multiplexers (cont.)

## Example chip: 8-to-1 MUX

 

(a) Connection diagram

 

(b) Logic symbol



# Multiplexers (cont.)


Efficient implementation: Majority function

Original truth table

A	B	C	F <sub>1</sub>
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

New truth table



A	B	F <sub>1</sub>
0	0	0
0	1	C
1	0	C
1	1	1

 

# Demultiplexers (DeMUX)
 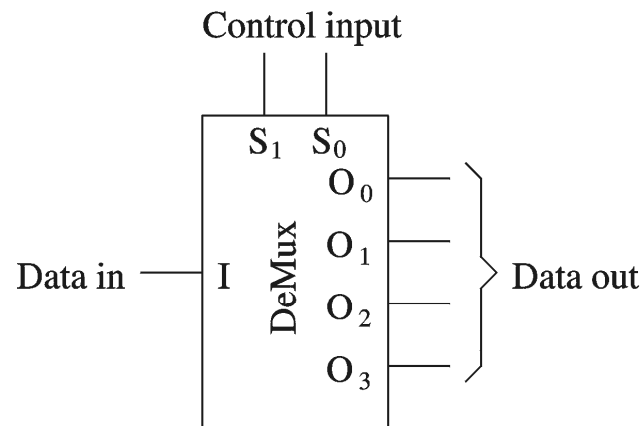
## ■ Demultiplexer



- a single input
- n selection inputs
- $2^n$  outputs



# Decoders

- Decoder selects one-out-of-N inputs


$I_1$	$I_0$	$O_3$	$O_2$	$O_1$	$O_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

  

# Decoders (cont.)


## Logic function implementation

A	B	C <sub>in</sub>	Sum	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

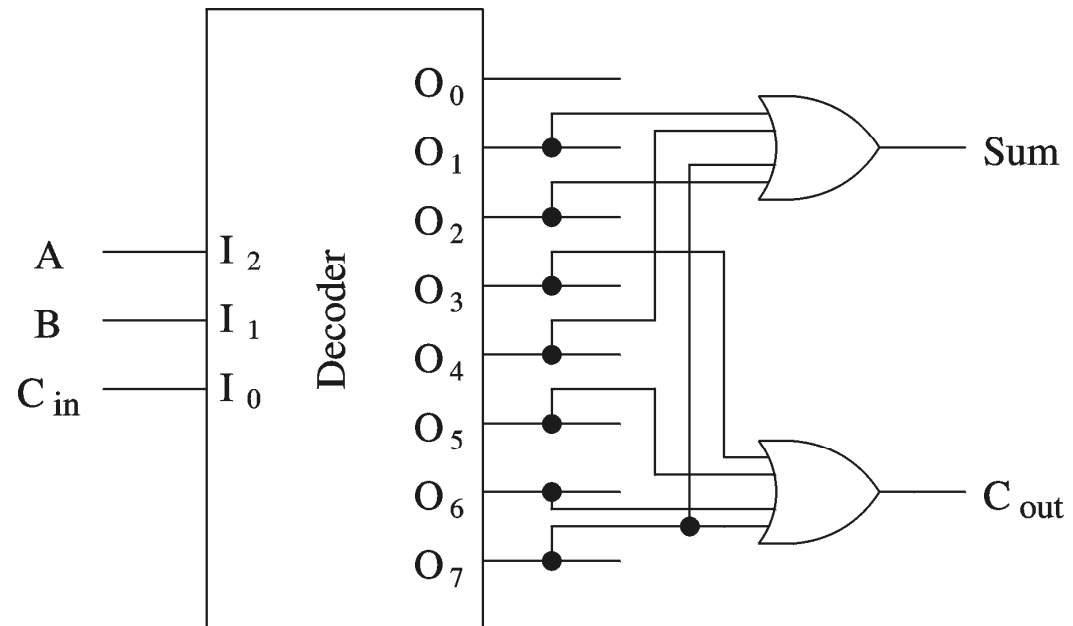
 
# Comparator


- Used to implement comparison operators ( $=$ ,  $>$ ,  $<$ ,  $\geq$ ,  $\leq$ )




# Comparator (cont.)

$$A=B: O_x = I_x (x=A<B, A=B, \& A>B)$$

## 4-bit magnitude comparator chip

 


(a) Connection diagram

 


(b) Logic symbol

# Comparator (cont.)
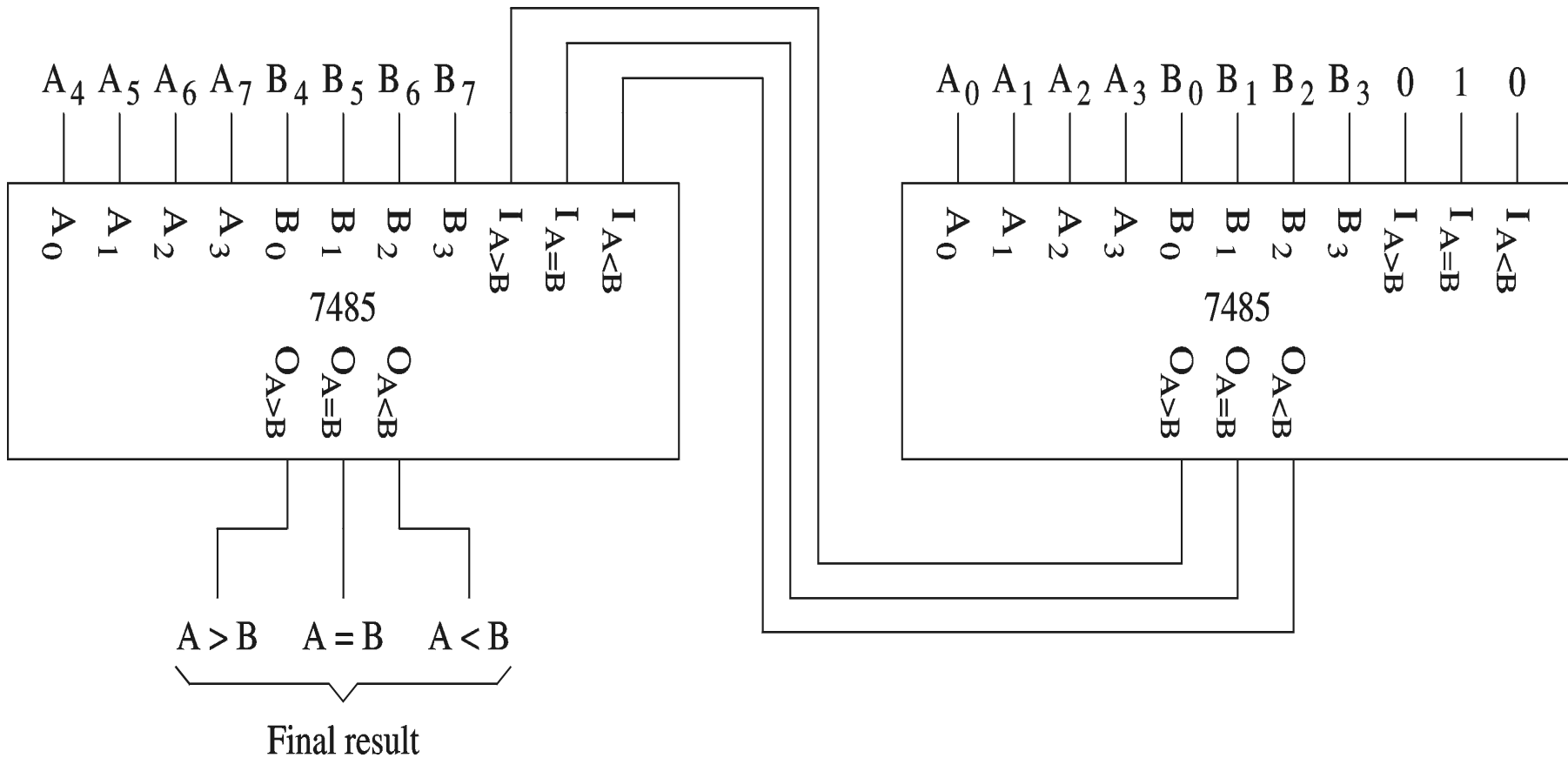
## Serial construction of an 8-bit comparator





# 1-bit Comparator

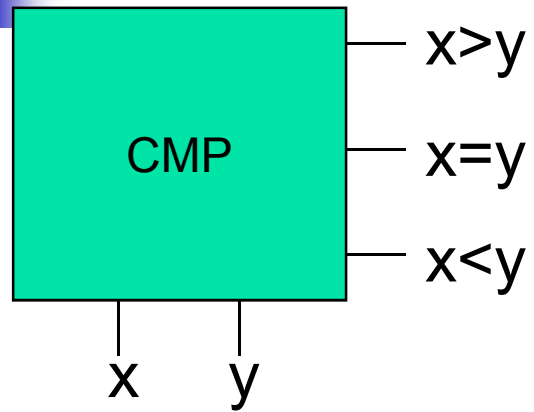

x	y	x>y	x=y	x<y



# 8-bit comparator

 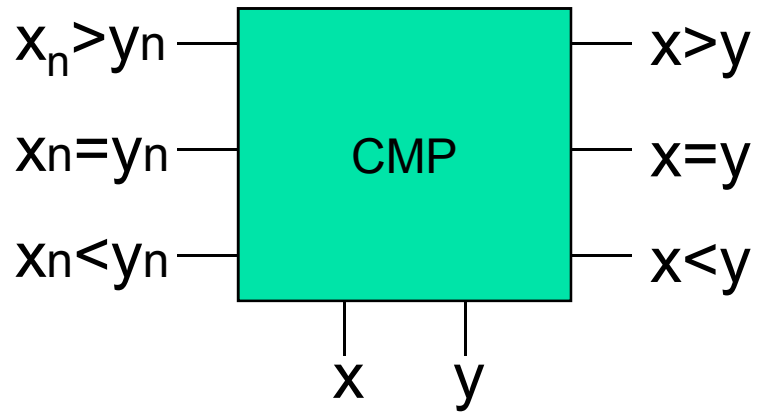



# Adders

---

- Half-adder


- Adds two bits
  - Produces a *sum* and *carry*
- Problem: Cannot use it to build larger inputs

- Full-adder

- Adds three 1-bit values
  - Like half-adder, produces a *sum* and *carry*
- Allows building N-bit adders
  - Simple technique
    - Connect  $C_{out}$  of one adder to  $C_{in}$  of the next
  - These are called *ripple-carry adders*


# Adders (cont.)

A	B	Sum	C <sub>out</sub>
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

(a) Half-adder truth table and implementation


A	B	C <sub>in</sub>	Sum	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

(b) Full-adder truth table and implementation

# Adders (cont.)

## A 16-bit ripple-carry adder

 



## Adders (cont.)

---

- Ripple-carry adders can be slow
  - Delay proportional to number of bits
- Carry lookahead adders
  - Eliminate the delay of ripple-carry adders
  - Carry-ins are generated independently
    - $C_0 = A_0 B_0$
    - $C_1 = A_0 B_0 A_1 + A_0 B_0 B_1 + A_1 B_1$
    - . . . .
  - Requires complex circuits
  - Usually, a combination carry lookahead and ripple-carry techniques are used



# Programmable Logic Arrays


---

- PLAs

- Implement sum-of-product expressions
  - No need to simplify the logical expressions
- Take  $N$  inputs and produce  $M$  outputs
  - Each input represents a logical variable
  - Each output represents a logical function output
- Internally uses
  - An AND array
    - Each AND gate receives  $2N$  inputs
      - $N$  inputs and their complements
  - An OR array


# Programmable Logic Arrays (cont.)

A blank PLA with 2 inputs and 2 outputs

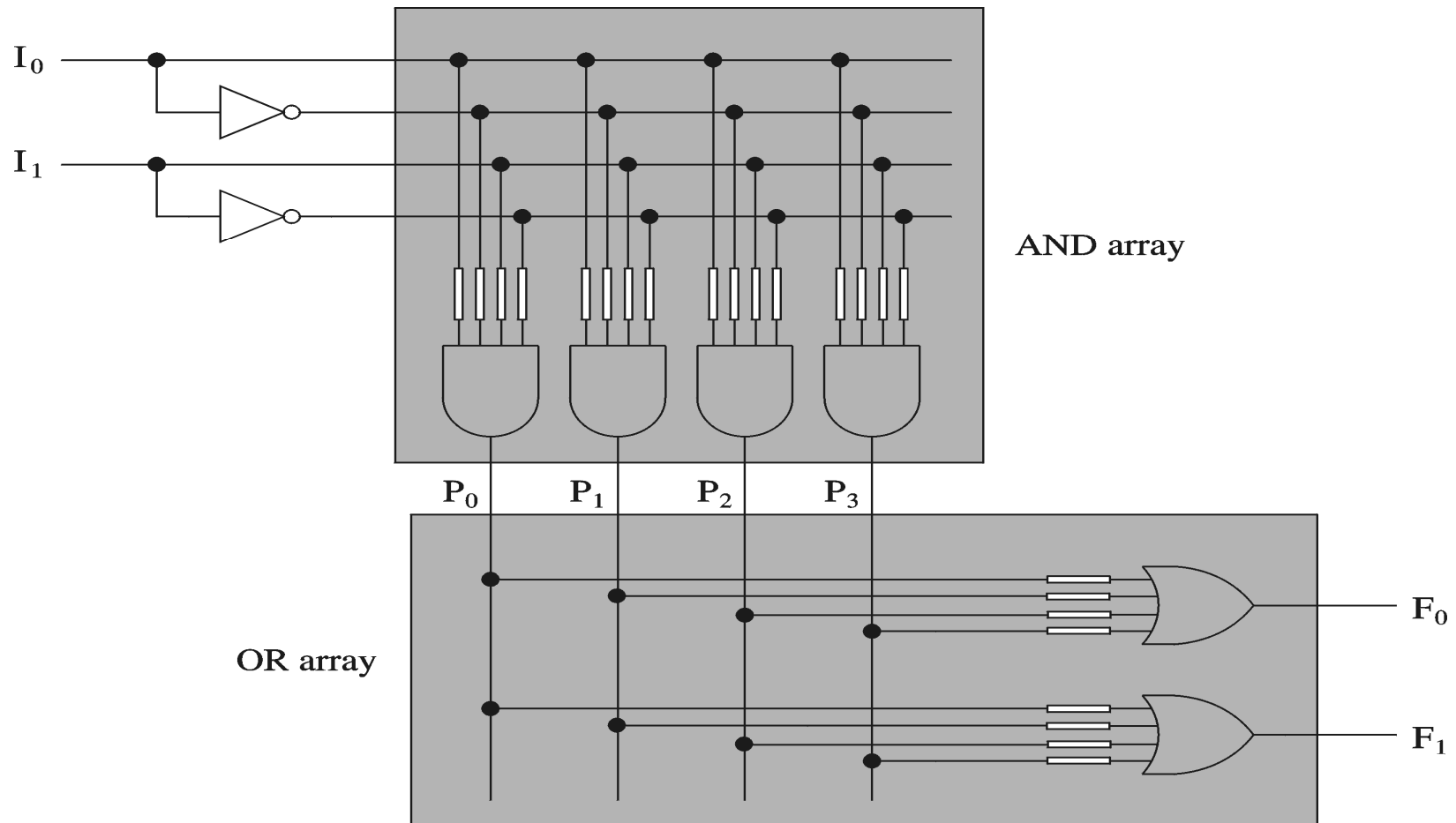

# Programmable Logic Arrays (cont.)


## Implementation examples

 




# Programmable Logic Arrays (cont.)

## Simplified notation

 


# 1-bit Arithmetic and Logic Unit

## Preliminary ALU design

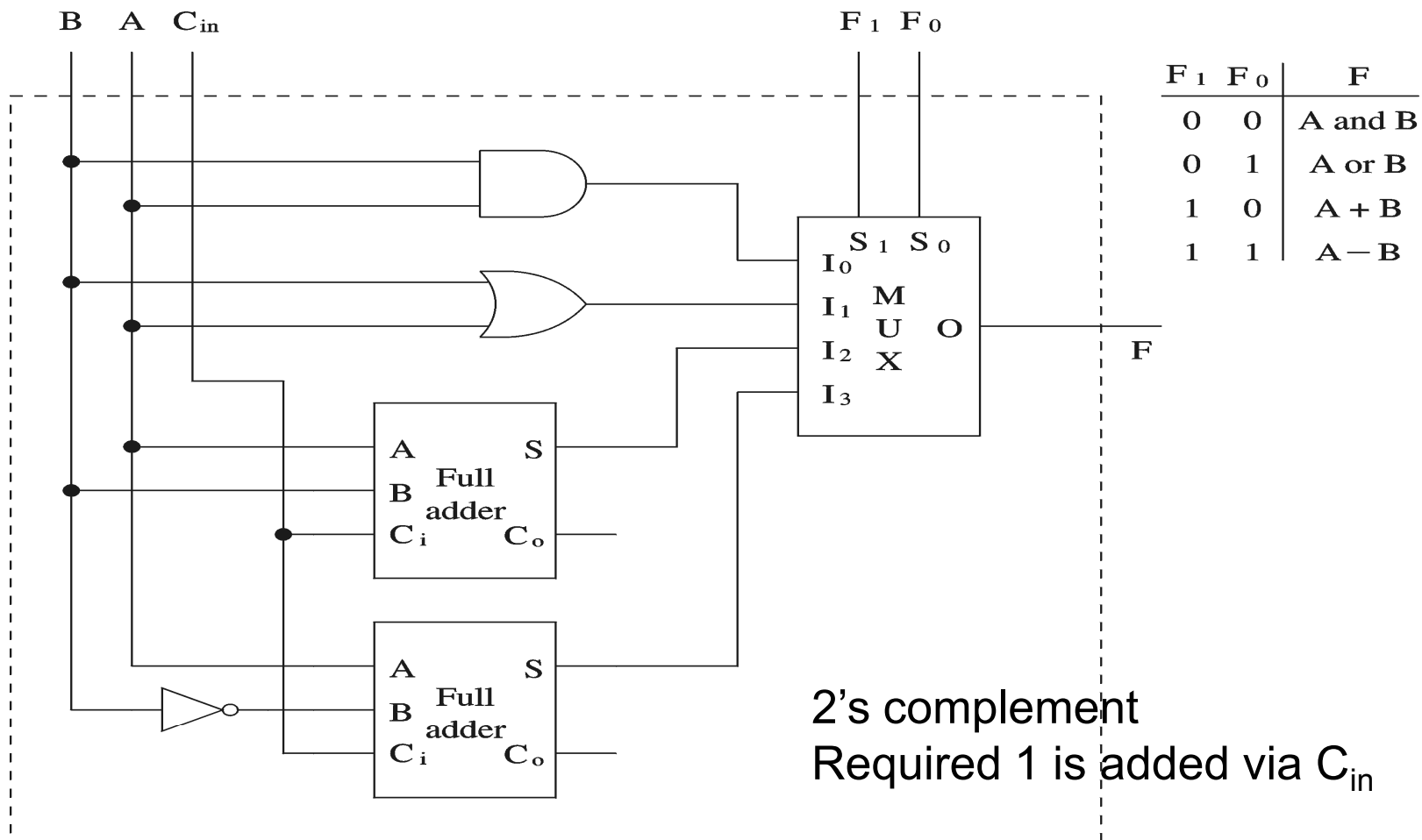


# 1-bit Arithmetic and Logic Unit (cont.)

## Final design

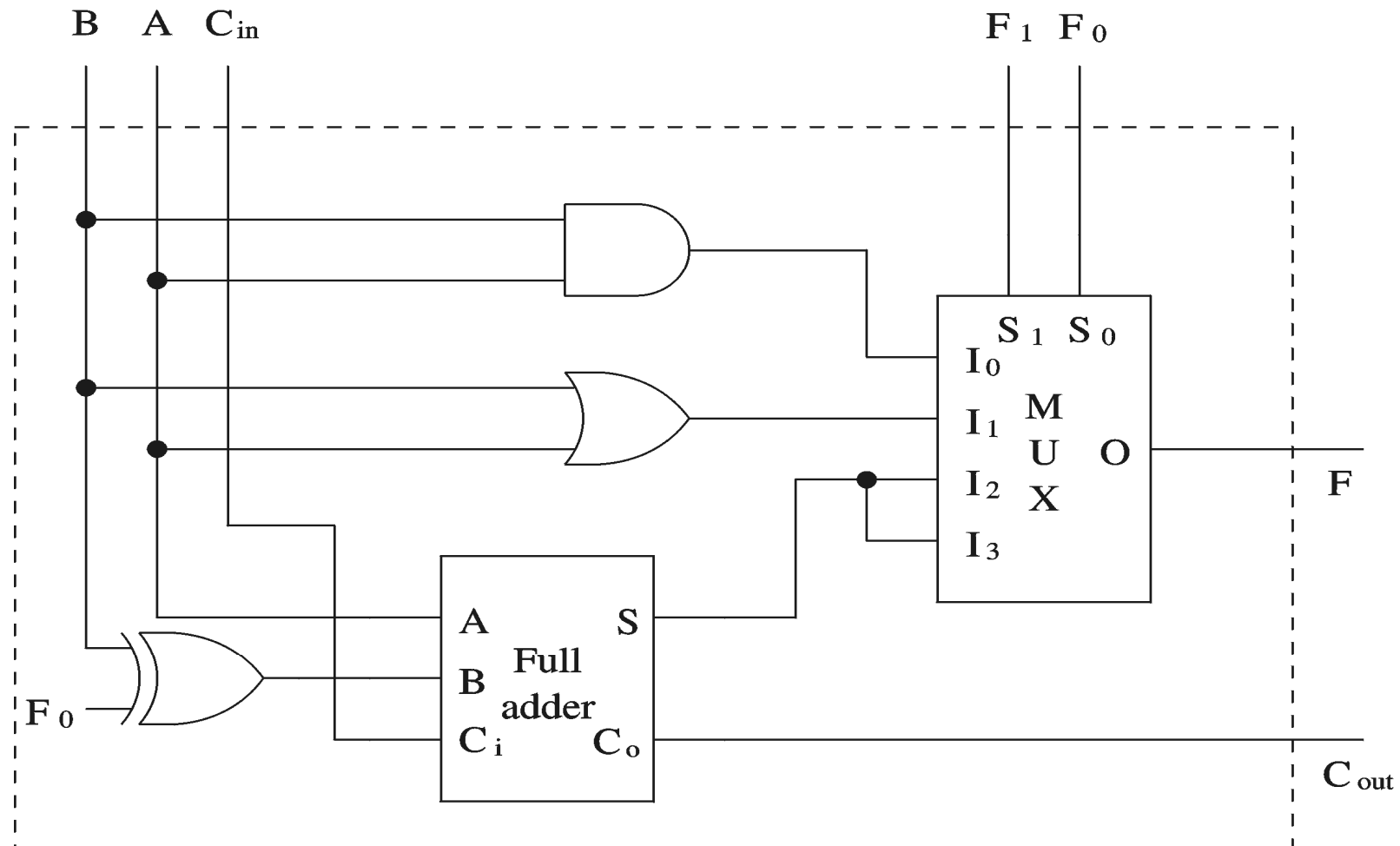


# Arithmetic and Logic Unit (cont.)

## 16-bit ALU

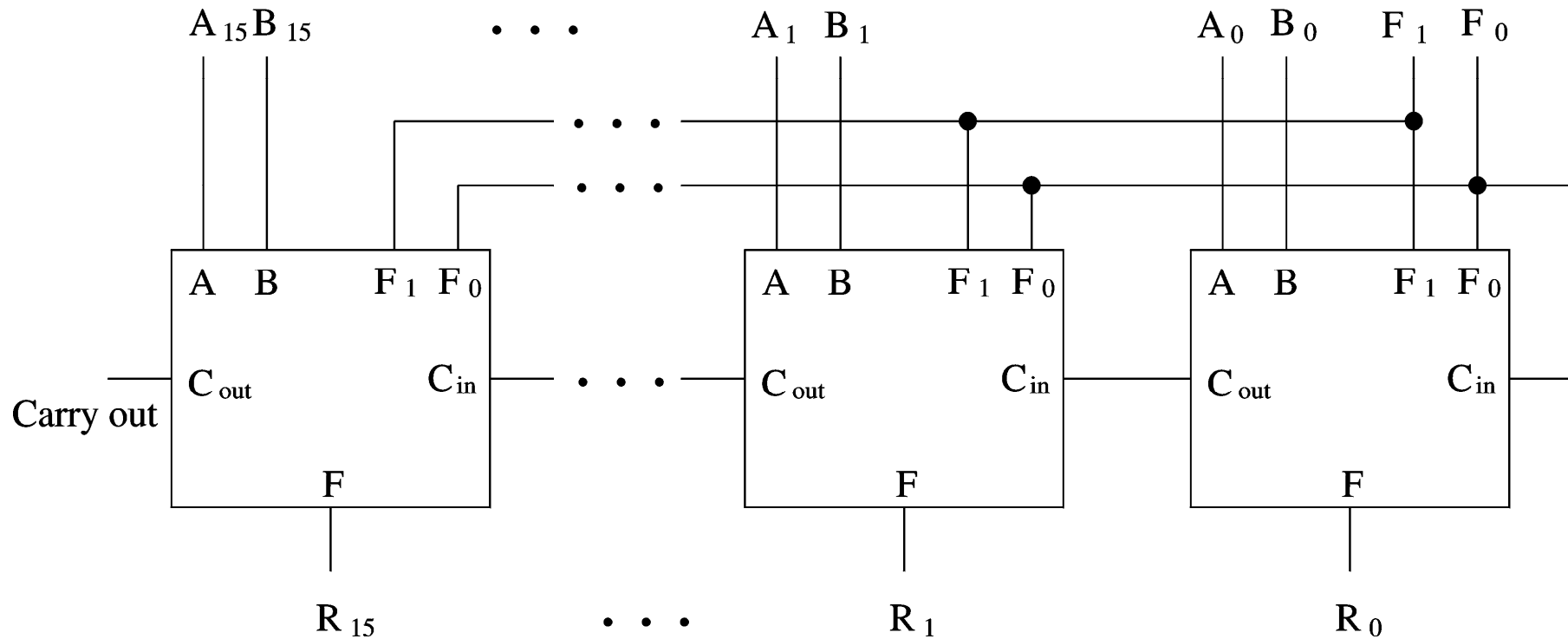


# Arithmetic and Logic Unit (cont'd)


## 4-bit ALU

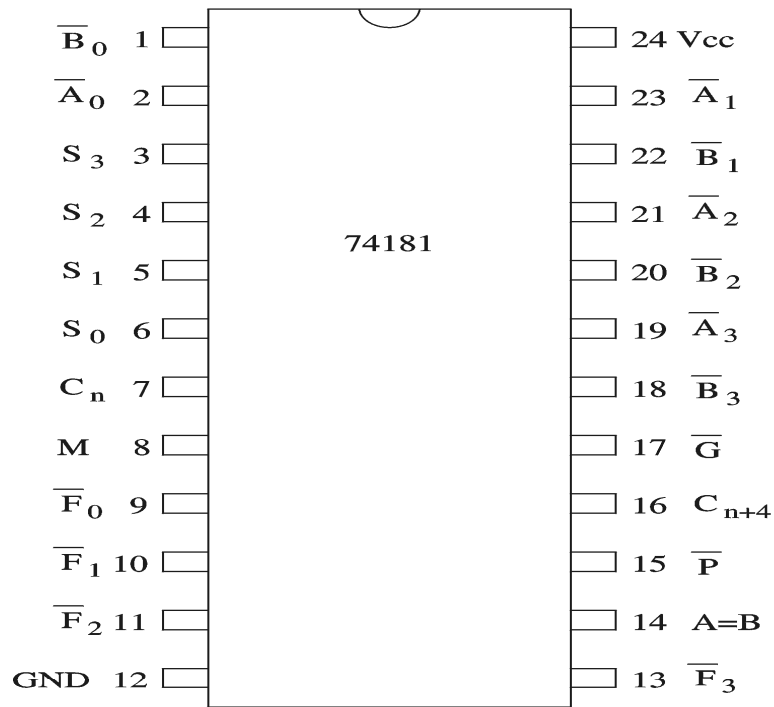

(a) Connection diagram

 

(b) Active low operands

 

(c) Active high operands




# Introduction to Sequential Circuits

---


- Output depends on current as well as past inputs
  - Depends on the history
  - Have “memory” property
- Sequential circuit consists of
  - Combinational circuit
  - Feedback circuit
  - Past input is encoded into a set of state variables
    - Uses feedback (to feed the state variables)
      - Simple feedback
      - Uses flip flops

# Introduction (cont.)

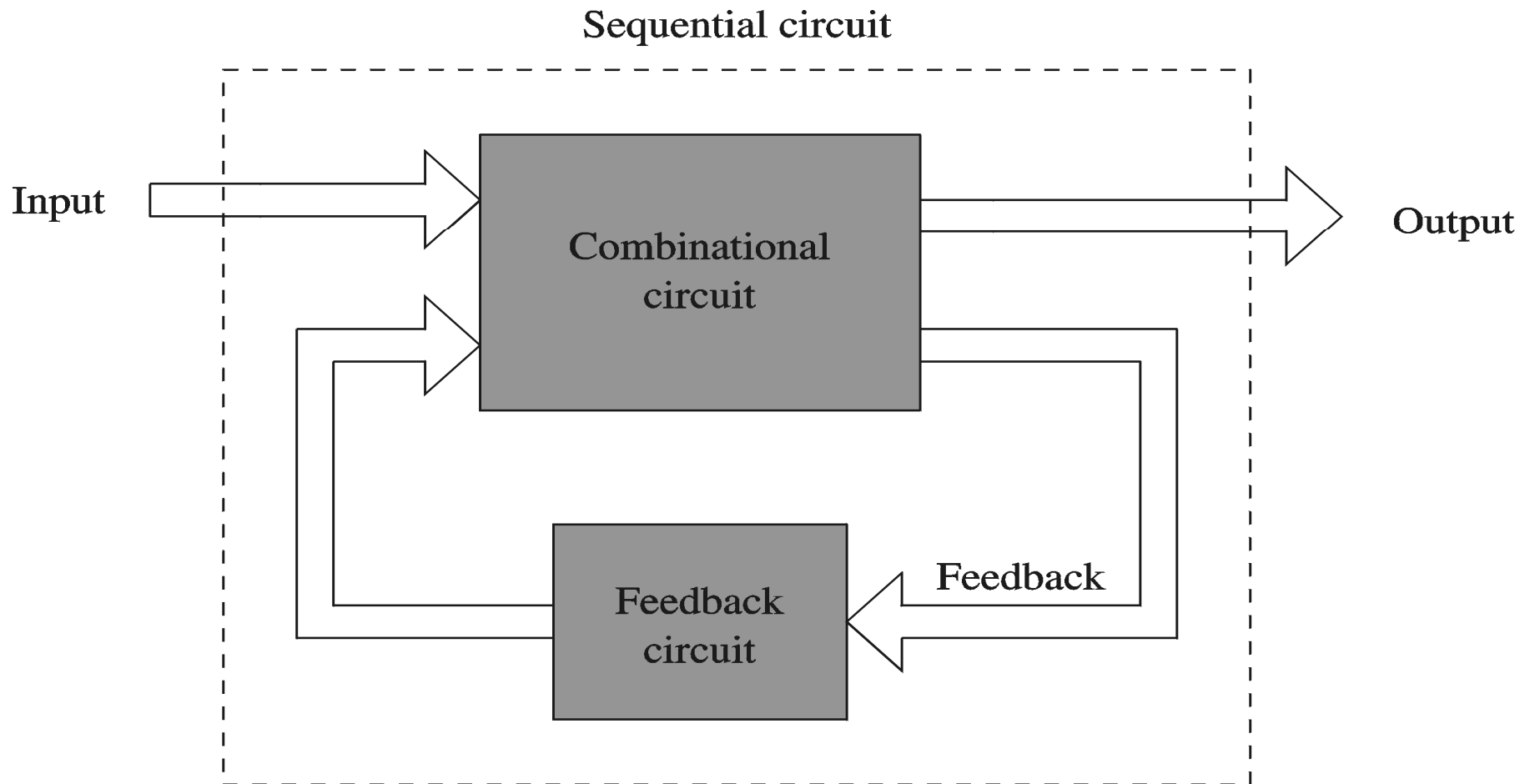
## Main components of a sequential circuit




# Clock Signal

 

(a) Symmetric

 

(b) Smaller ON period

 

(c) Smaller OFF period






## Clock Signal (cont.)


---

- Clock serves two distinct purposes
  - Synchronization point
    - Start of a cycle
    - End of a cycle
    - Intermediate point at which the clock signal changes levels
  - Timing information
    - Clock period, ON, and OFF periods
- Propagation delay
  - Time required for the output to react to changes in the inputs

# Clock Signal (cont.)

 

(a) Circuit diagram

 


(b) Timing diagram


# SR Latches

- Can remember a bit
- Level-sensitive (not edge-sensitive)

A NOR gate implementation of SR latch

 

(a) Circuit diagram

 


(b) Logic symbol

S	R	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
<del>1</del>	<del>1</del>	<del>0</del>


(c) Truth table
 
# SR Latches (cont.)

- SR latch outputs follow inputs
- In clocked SR latch, outputs respond at specific instances
  - Uses a clock signal




(a) Circuit diagram

 


(b) Logic symbol

# D Latches

- D Latch
  - Avoids the SR = 11 state

 

(a) Circuit diagram

 


(b) Logic symbol

D	$Q_{n+1}$
0	0
1	1


(c) Truth table
 
# Positive Edge-Triggered D Flip-Flops

- Edge-sensitive devices
  - Changes occur either at positive or negative edges



(a) Circuit diagram

 


(b) Logic symbol

# Notation for Latches & Flip-Flops


- Not strictly followed in the literature

Latches


Flip-flops

 


(a)  
Low level

 

(b)  
High level

 


(c)  
Positive edge

 


(d)  
Negative edge

# Example of Shift Register Using D Flip-Flops

74164 shift  
Register chip

 

(a) Connection diagram

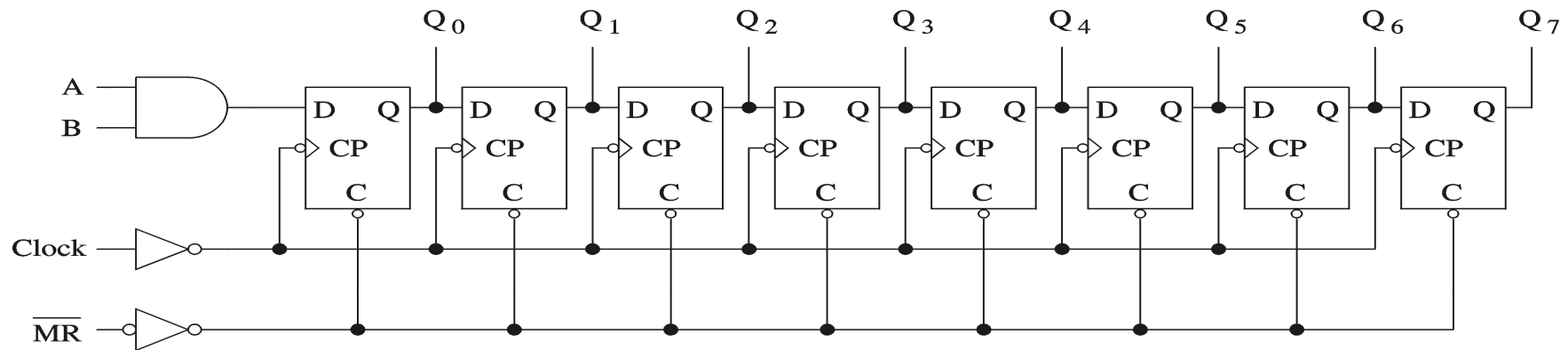


(b) Logic diagram



# Memory Design Using D Flip-Flops



Require separate data in and out lines

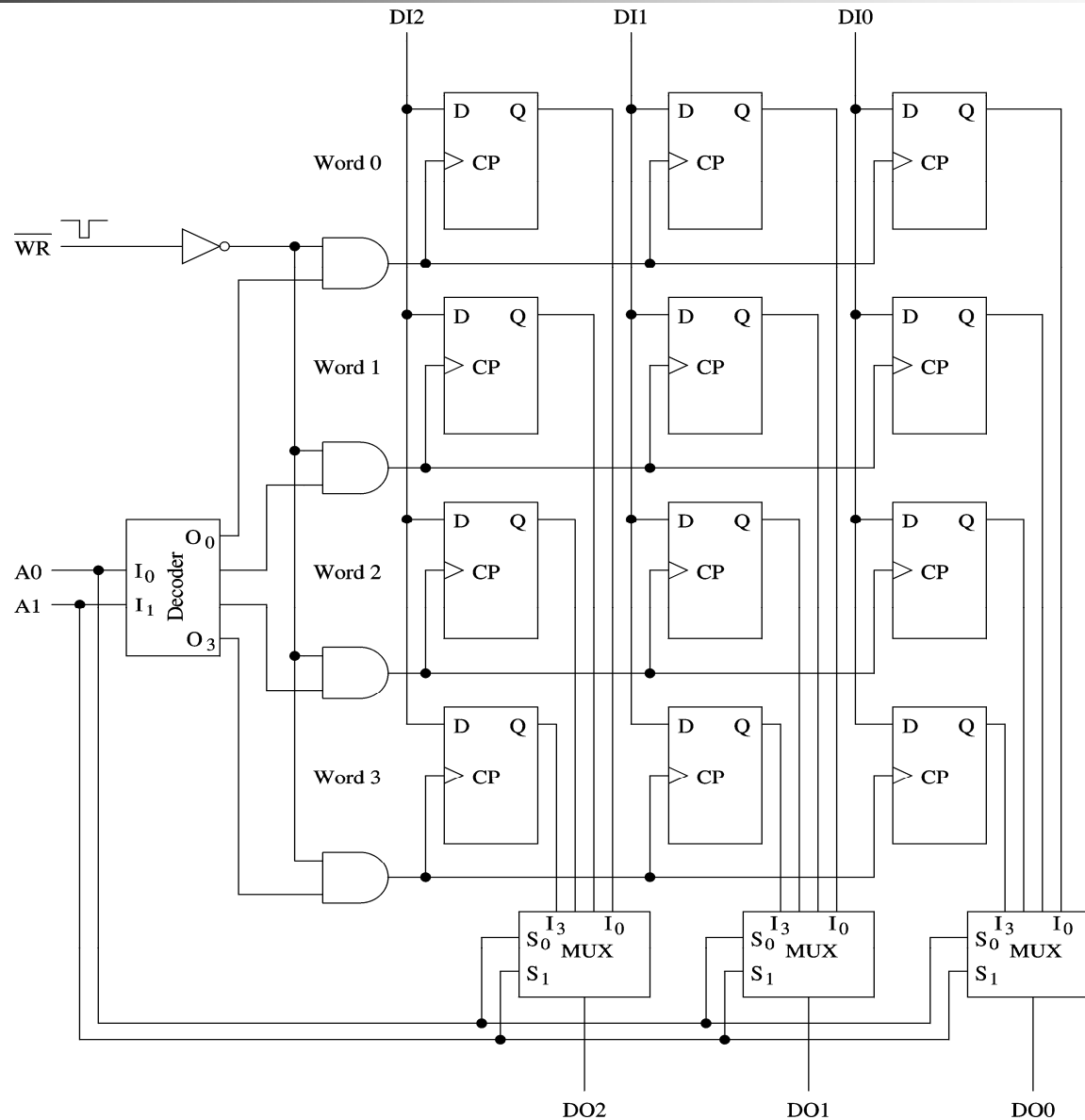

# JK Flip-Flops

JK flip-flop  
(master-slave)

J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$Q_n$

 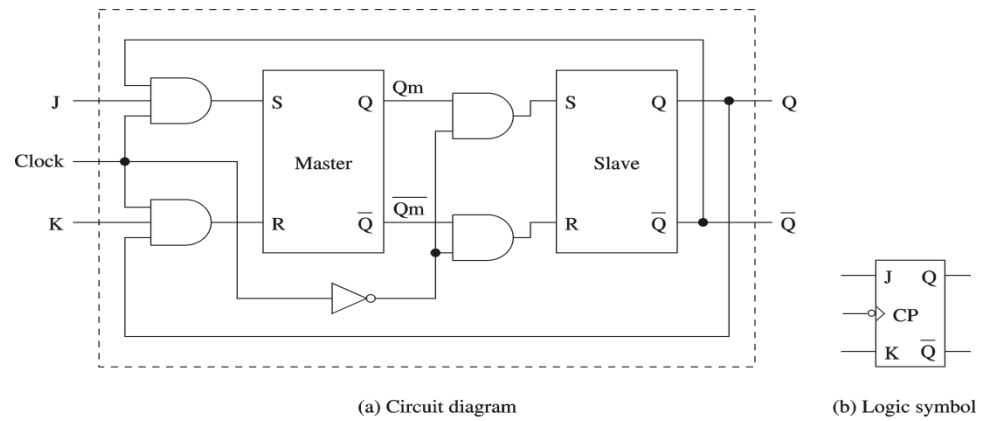


(c) Timing diagram

# Examples of D & JK Flip-Flops


## Two example chips

### D latches

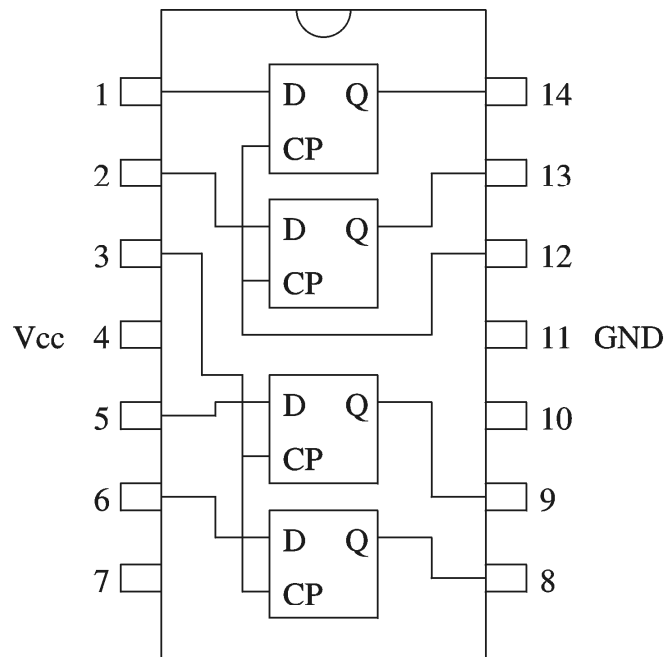

(a) 7477

### JK flip-flops

 


(b) 7476

# Example of Shift Register Using JK Flip-Flops

- Shift Registers

- Can shift data left or right with each clock pulse
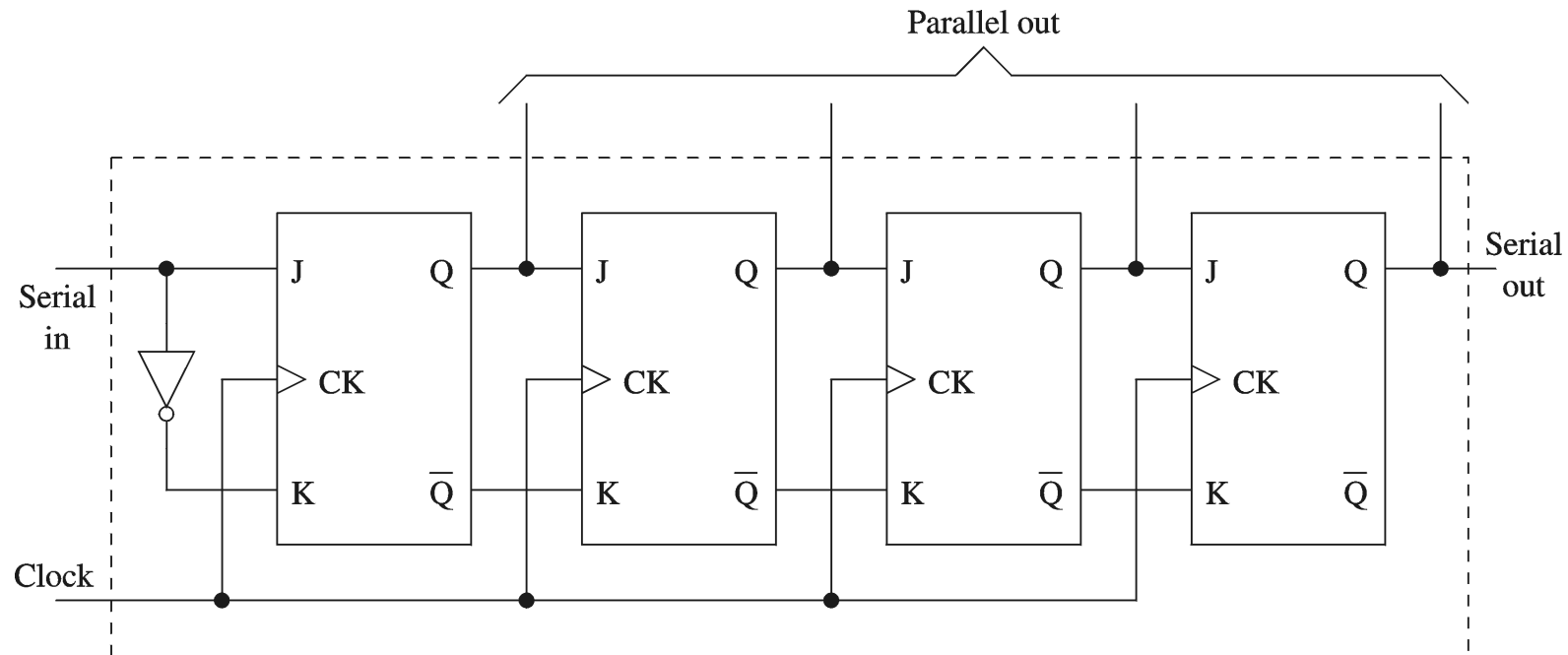
## A 4-bit shift register using JK flip-flops





# Example of Counter Using JK Flip-Flops

---

- Counters

- Easy to build using JK flip-flops

- Use the JK = 11 to toggle

- Binary counters

- Simple design

- B bits can count from 0 to  $2^B - 1$

- Ripple counter

- Increased delay as in ripple-carry adders

- Delay proportional to the number of bits


- Synchronous counters

- Output changes more or less simultaneously


- Additional cost/complexity

# Modulo-8 Binary Ripple Counter Using JK Flip-Flops

LSB

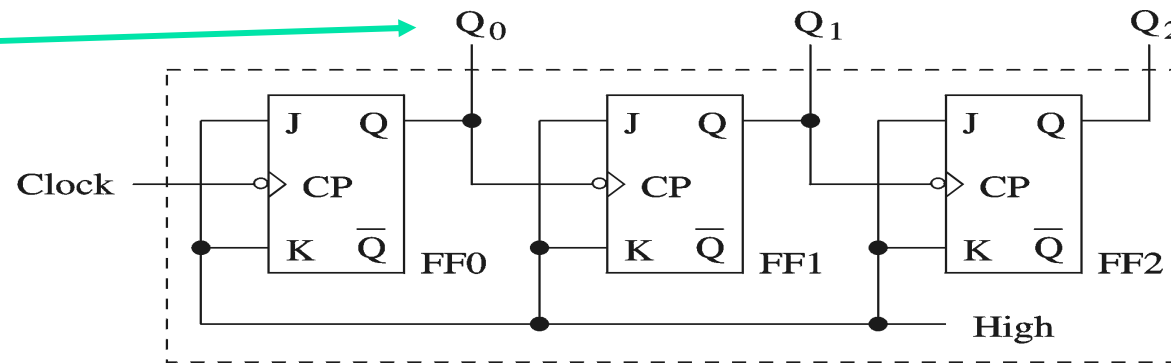


(a) Circuit diagram

 


(b) Timing diagram
 
# Synchronous Modulo-8 Counter


- Designed using the following simple rule
  - Change output if the preceding count bits are 1
    - Q1 changes whenever  $Q_0 = 1$
    - Q2 changes whenever  $Q_1Q_0 = 11$




# Example Counters

 


(a) Connection diagram

 

(b) Logic symbol

 

(c) State diagram of 74161

 

(d) State diagram of 74160





# Sequential Circuit Design

---

- Sequential circuit consists of
  - A combinational circuit that produces output
  - A feedback circuit
    - We use JK flip-flops for the feedback circuit
- Simple counter examples using JK flip-flops
  - Provides alternative counter designs
  - We know the output
    - Need to know the input combination that produces this output
    - Use an excitation table
      - Built from the truth table



# Sequential Circuit Design (cont.)

(a) JK flip-flop truth table

J	K	$Q_n$	$Q_{n+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

(b) Excitation table for JK flip-flops

$Q_n$	$Q_{n+1}$	J	K
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0



## Sequential Circuit Design (cont.)

---

- Build a design table that consists of
  - Current state output
  - Next state output
  - JK inputs for each flip-flop
- Binary counter example
  - 3-bit binary counter
  - 3 JK flip-flops are needed
  - Current state and next state outputs are 3 bits each
  - 3 pairs of JK inputs



# Sequential Circuit Design (cont.)

## Design table for the binary counter example

Present state			Next state			JK flip-flop inputs					
A	B	C	A	B	C	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>
0	0	0	0	0	1	0	d	0	d	1	d
0	0	1	0	1	0	0	d	1	d	d	1
0	1	0	0	1	1	0	d	d	0	1	d
0	1	1	1	0	0	1	d	d	1	d	1
1	0	0	1	0	1	d	0	0	d	1	d
1	0	1	1	1	0	d	0	1	d	d	1
1	1	0	1	1	1	d	0	d	0	1	d
1	1	1	0	0	0	d	1	d	1	d	1

# Sequential Circuit Design (cont.)

Use K-maps to simplify expressions for JK inputs

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	d	d	d	d

$$J_A = B C$$

		BC			
		00	01	11	10
A	0	d	d	d	d
	1	0	0	1	0

$$K_A = B C$$

		BC			
		00	01	11	10
A	0	0	1	d	d
	1	0	1	d	d

$$J_B = C$$

		BC			
		00	01	11	10
A	0	d	d	1	0
	1	d	d	1	0

$$K_B = C$$

		BC			
		00	01	11	10
A	0	1	d	d	1
	1	1	d	d	1


$$J_C = 1$$

		BC			
		00	01	11	10
A	0	d	1	1	d
	1	d	1	1	d

$$K_C = 1$$
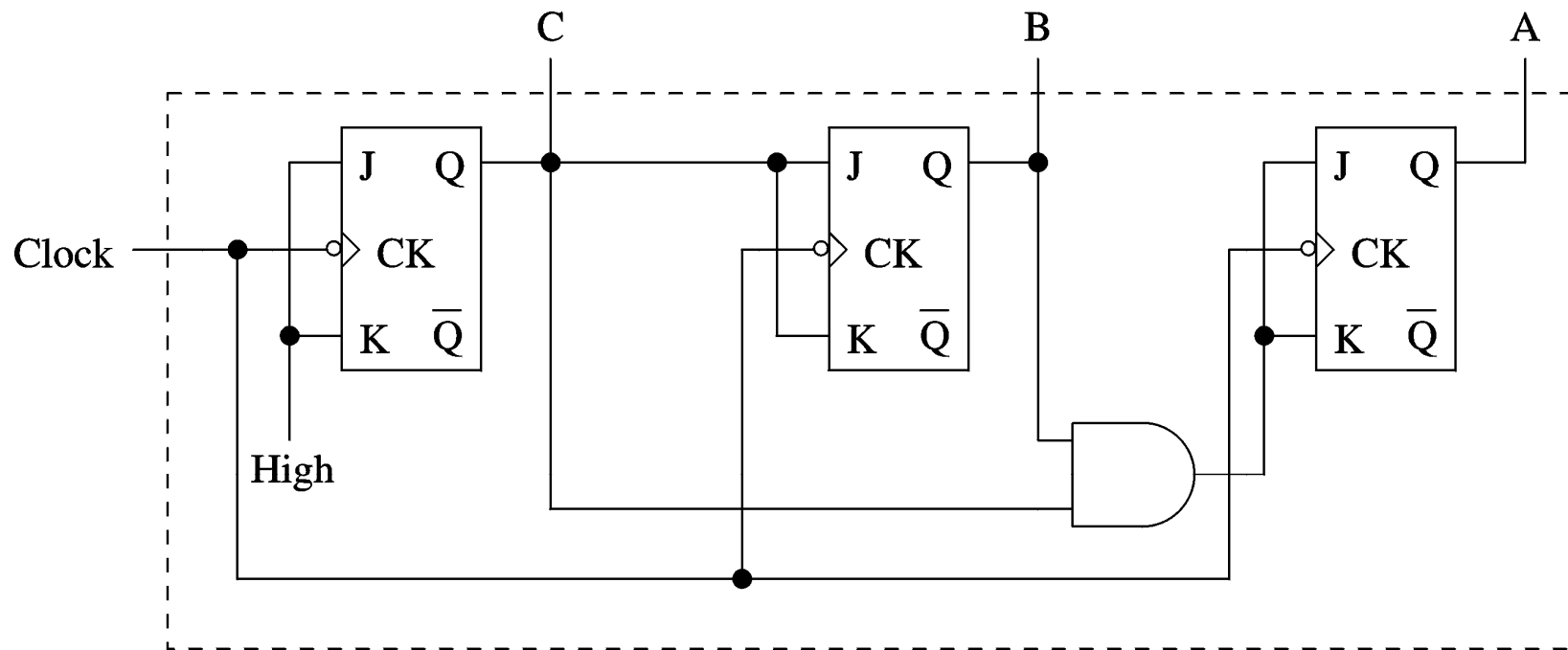
# Sequential Circuit Design (cont.)

- Final circuit for the binary counter example
  - Compare this design with the synchronous counter design




# Sequential Circuit Design (cont.)

- A more general counter design
  - Does not step in sequence

0 → 3 → 5 → 7 → 6 → 0

 - Same design process
- One significant change
  - Missing states
    - 1, 2, and 4
    - Use don't cares for these states



# Sequential Circuit Design (cont.)

Design table  
for the  
general  
counter  
example

Present state			Next state			JK flip-flop inputs					
A	B	C	A	B	C	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>
0	0	0	0	1	1	0	d	1	d	1	d
0	0	1	—	—	—	d	d	d	d	d	d
0	1	0	—	—	—	d	d	d	d	d	d
0	1	1	1	0	1	1	d	d	1	d	0
1	0	0	—	—	—	d	d	d	d	d	d
1	0	1	1	1	1	d	0	1	d	d	0
1	1	0	0	0	0	d	1	d	1	0	d
1	1	1	1	1	0	d	0	d	0	d	1



# Sequential Circuit Design (cont.)

K-maps to simplify JK input expressions

	BC	00	01	11	10
A	0	0	d	1	d
	1	d	d	d	d

$$J_A = B$$

	BC	00	01	11	10
A	0	d	d	d	d
	1	d	0	0	1

$$K_A = \bar{C}$$

	BC	00	01	11	10
A	0	1	d	d	d
	1	d	1	d	d

$$J_B = 1$$

	BC	00	01	11	10
A	0	d	d	1	d
	1	d	d	0	1

$$K_B = \bar{A} + \bar{C}$$

	BC	00	01	11	10
A	0	1	d	d	d
	1	d	d	d	0


$$J_C = \bar{A}$$

	BC	00	01	11	10
A	0	d	d	0	d
	1	d	0	1	d

$$K_C = AB$$
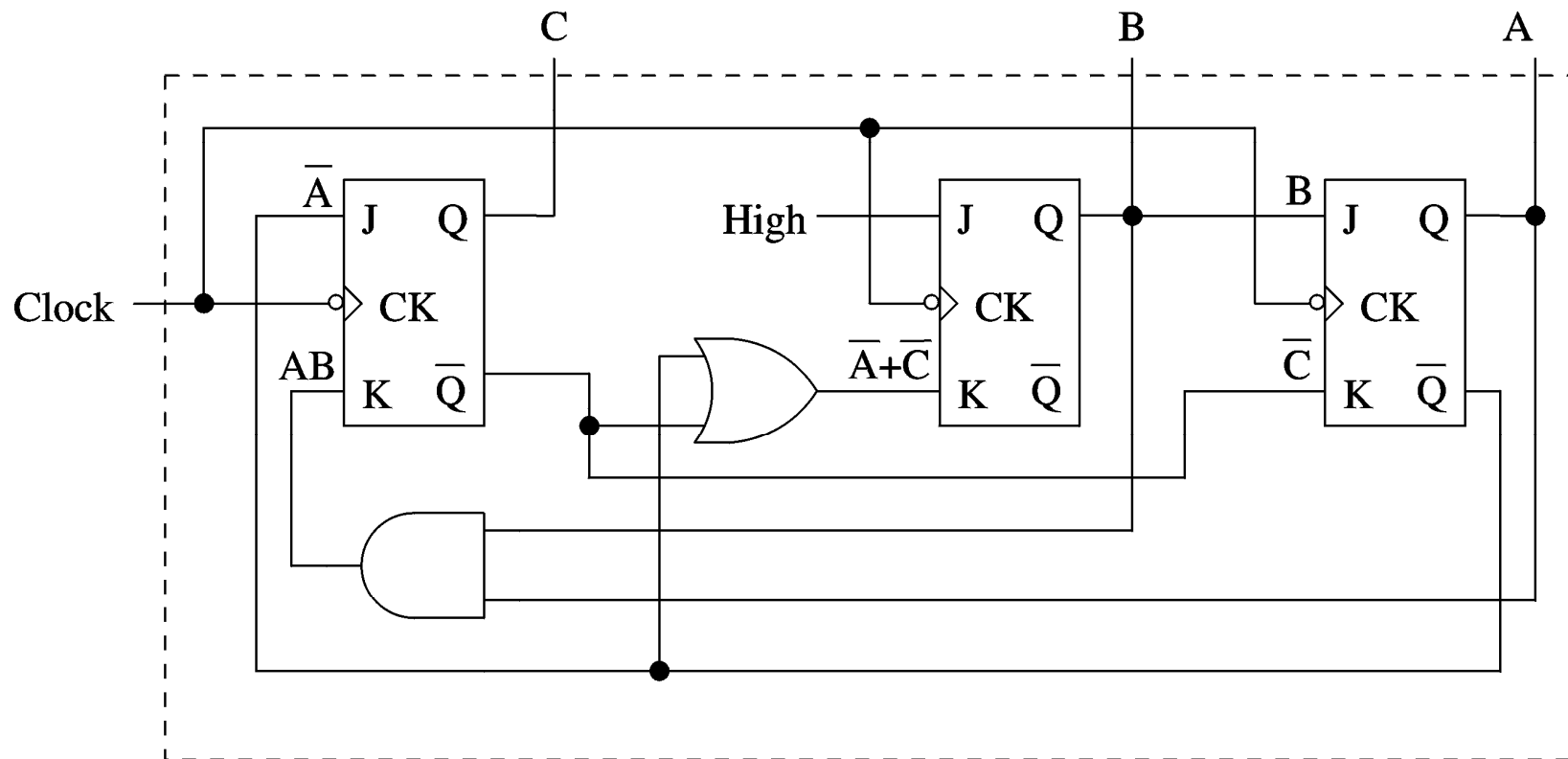
# Sequential Circuit Design (cont.)

Final circuit for the general counter example






# General Design Process

---

- FSM can be used to express the behavior of a sequential circuit
  - Counters are a special case
  - State transitions are indicated by arrows with labels X/Y
    - X: inputs that cause system state change
    - Y: output generated while moving to the next state
- Look at two examples
  - Even-parity checker
  - Pattern recognition
 
# General Design Process (cont.)

- Even-parity checker
  - FSM needs to remember one of two facts
    - Number of 1's is odd or even
    - Need only two states
      - 0 input does not change the state
      - 1 input changes state
  - Simple example
    - Complete the design as an exercise






# General Design Process (cont.)

---

- Pattern recognition example
  - Outputs 1 whenever the input bit sequence has exactly two 0s in the last three input bits
  - FSM requires three special states to during the initial phase
    - S0 – S2
  - After that we need four states
    - S3: last two bits are 11
    - S4: last two bits are 01
    - S5: last two bits are 10
    - S6: last two bits are 00
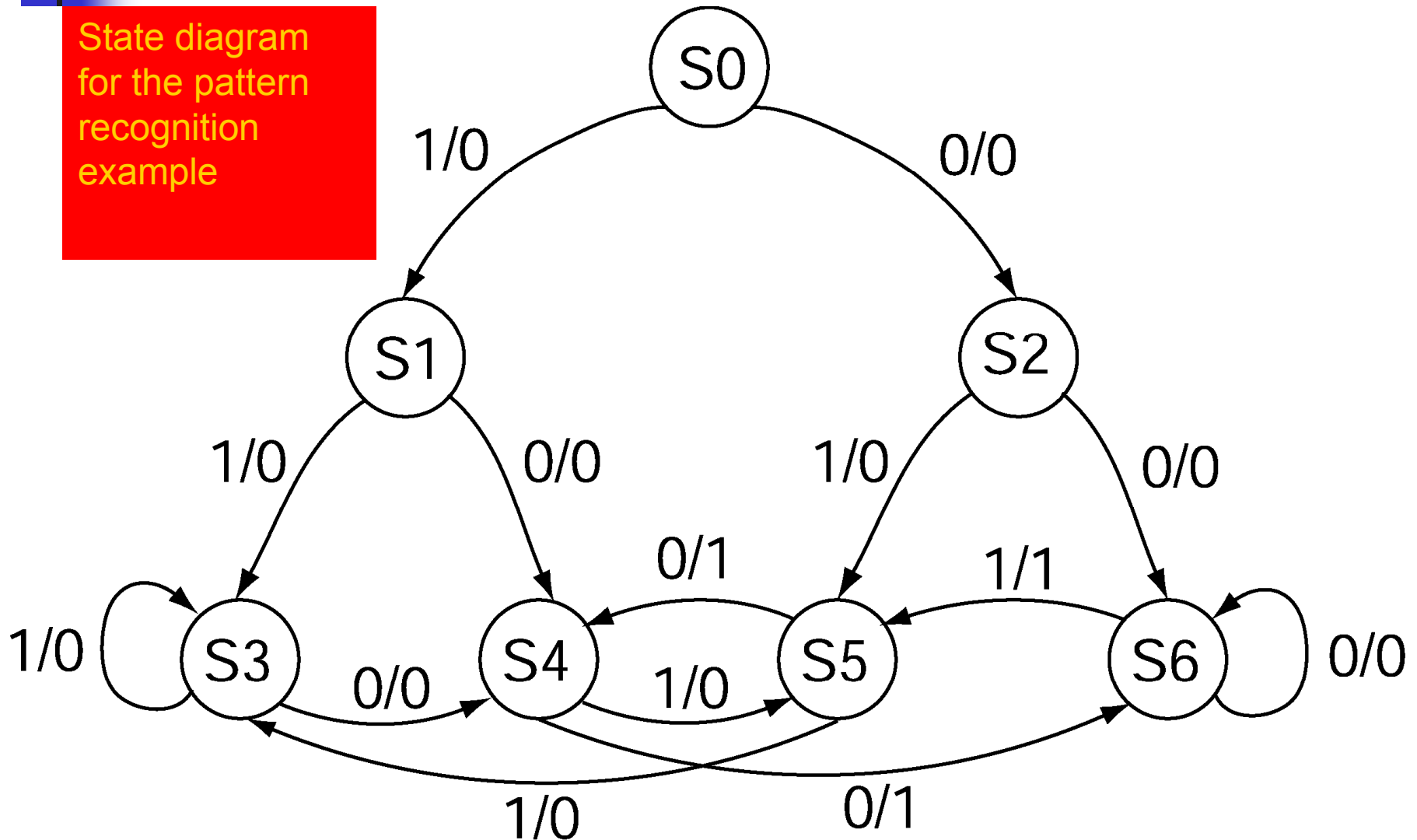
# General Design Process (cont.)

State diagram  
for the pattern  
recognition  
example





# General Design Process (cont.)

---

- Steps in the design process
  1. Derive FSM
  2. State assignment
    - \* Assign flip-flop states to the FSM states
      - \* Necessary to get an efficient design
  3. Design table derivation
    - \* Derive a design table corresponding to the assignment in the last step
  4. Logical expression derivation
    - \* Use K-maps as in our previous examples
  5. Implementation



# General Design Process (cont.)

---

- State assignment

- Three heuristics

- Assign adjacent states for

- states that have the same next state
- states that are the next states of the same state
- States that have the same output for a given input

- For our example

- Heuristic 1 groupings:  $(S1, S3, S5)^2 (S2, S4, S6)^2$
- Heuristic 2 groupings:  $(S1, S2) (S3, S4)^3 (S5, S6)^3$
- Heuristic 1 groupings:  $(S4, S5)$





# General Design Process (cont.)

State table for the  
pattern  
recognition  
example

Present state	Next state		Output	
	X = 0	X = 1	X = 0	X = 1
S0	S2	S1	0	0
S1	S4	S3	0	0
S2	S6	S5	0	0
S3	S4	S3	0	0
S4	S6	S5	1	0
S5	S4	S3	1	0
S6	S6	S5	0	1

# General Design Process (cont.)

## K-map for state assignment

		BC			
		00	01	11	10
A	0	S0	S3	S5	S1
	1		S4	S6	S2

## State assignment

State		A	B	C
S0	=	0	0	0
S1	=	0	1	0
S2	=	1	1	0
S3	=	0	0	1
S4	=	1	0	1
S5	=	0	1	1
S6	=	1	1	1

# General Design Process (cont.)

Design table

Present state			Present state	Next state			Present state	JK flip-flop inputs					
A	B	C	X	A	B	C	Y	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>
0	0	0	0	1	1	0	0	1	d	1	d	0	d
0	0	0	1	0	1	0	0	0	d	1	d	0	d
0	0	1	0	1	0	1	0	1	d	0	d	d	0
0	0	1	1	0	0	1	0	0	d	0	d	d	0
0	1	0	0	1	0	1	0	1	d	d	1	1	d
0	1	0	1	0	0	1	0	0	d	d	1	1	d
0	1	1	0	1	0	1	1	1	d	d	1	d	0
0	1	1	1	0	0	1	0	0	d	d	1	d	0
1	0	1	0	1	1	1	1	1	0	1	d	d	0
1	0	1	1	0	1	1	0	0	1	1	d	d	0
1	1	0	0	1	1	1	0	0	0	d	0	1	d
1	1	0	1	0	1	1	0	0	1	d	0	1	d
1	1	1	0	1	1	1	0	0	0	d	0	d	0
1	1	1	1	0	1	1	1	0	1	d	0	d	0

# General Design Process (cont.)

		CX			
AB		00	01	11	10
00		1	0	0	1
01		1	0	0	1
11		d	d	d	d
10		d	d	d	d

$$J_A = \bar{X}$$

		CX			
AB		00	01	11	10
00		d	d	d	d
01		d	d	d	d
11		0	1	1	0
10		d	d	1	0

$$K_A = X$$

K-maps for JK inputs

		CX			
AB		00	01	11	10
00		1	1	0	0
01		d	d	d	d
11		d	d	d	d
10		d	d	1	1

$$J_B = \bar{C} + A$$

		CX			
AB		00	01	11	10
00		d	d	d	d
01		1	1	1	1
11		0	0	0	0
10		d	d	d	d

$$K_B = \bar{A}$$

K-map for the output

		CX			
AB		00	01	11	10
00		0	0	d	d
01		1	1	d	d
11		1	1	d	d
10		d	d	d	d

$$J_C = B$$


		CX			
AB		00	01	11	10
00		d	d	0	0
01		d	d	0	0
11		d	d	0	0
10		d	d	0	0

$$K_C = 0$$

		CX			
AB		00	01	11	10
00		0	0	0	0
01		0	0	0	1
11		0	0	1	0
10		d	d	0	1


$$Y = \bar{A}BC\bar{X} + ABCX + A\bar{B}\bar{X}$$

# General Design Process (cont.)

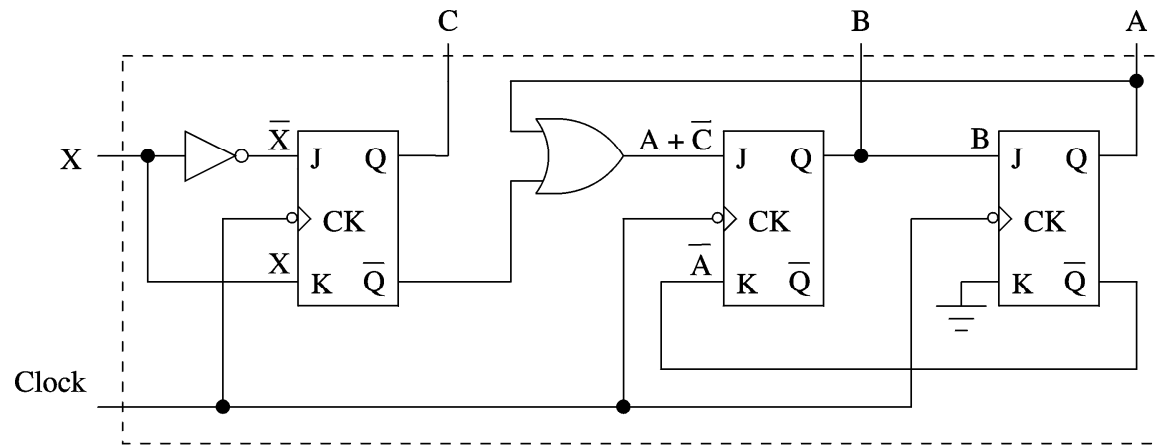

(a)

Final implementation

 

(b)

